

3.7 4T, 2个N沟道MOS晶体管 2个P沟道MOS晶体管

3.10 扇入：在特定逻辑系列中，门电路所具有的输入端的数目


扇出：逻辑门电路在不超过其最坏情况负载规格的条件下，能够驱动的输入端个数

扇出是必须计算的，因为扇出要保证不超过最坏情况负载规格

3.11	A	B	C	D	Q ₁	Q ₂	Q ₃	Q ₄	Q ₇	Q ₆	Q ₅	Q ₈	Z
	L	L	L	L	off	on	off	on	off	on	off	on	H
	L	L	L	H	off	on	off	on	off	on	on	off	L
	L	L	H	L	off	on	off	on	on	off	off	on	L
	L	L	H	H	off	on	off	on	on	off	on	off	L
	L	H	L	L	off	on	on	off	off	on	off	on	H
	L	H	L	H	off	on	on	off	off	on	on	off	L
	L	H	H	L	off	on	on	off	on	off	off	on	L
	L	H	H	H	off	on	on	off	on	off	on	off	L
	H	L	L	L	on	off	off	on	off	on	off	on	H
	H	L	L	H	on	off	off	on	off	on	on	off	L
	H	L	H	L	on	off	off	on	on	off	off	on	L
	H	L	H	H	on	off	off	on	on	off	on	off	L
	H	H	L	L	on	off	on	off	off	on	off	on	L
	H	H	L L	H	on	off	on	off	off	on	on	off	L
	H	H	H	L	on	off	on	off	on	off	of	on	L
	H	H	H	H	on	off	on	off	on	off	on	off	L


 
$$Z = \overline{(A \wedge B) \vee (C \vee D)}$$



3.20 $V_{IHmin} = 3.15V$ $V_{ILmax} = 1.35V$, $V_{CC} = 4.5V$, 假设输出与电阻性负载相连

当 $V_{CC} = V_{CCmin}$, $V_{IN} = V_{IH}$, $I_{OL} = 4mA$ 时, $V_{OLmax} = 0.33V$

当 $V_{CC} = V_{CCmin}$, $V_{IN} = V_{IL}$, $I_{OH} = -4mA$ 时, $V_{OHmin} = 3.84V$

∴ 低态直流噪声容限为 $1.35 - 0.33 = 1.02V$

高态直流噪声容限为 $3.84 - 3.15 = 0.69V$

3.22 $V_{IHmin} = 3.15V$

$V_{ILmax} = 1.35V$

$I_{IHmax} = 1\mu A$, 所需假设: $V_{CC} = 5.5V$, $V_I = 5.5V$

$I_{ILmax} = -1\mu A$, 所需假设: $V_{CC} = 5.5V$, $V_I = 0V$

$V_{OHmin} = 3.84V$ 所需假设: $V_{CC} = 4.5V$, $V_{IN} = V_{IL}$, $I_{OH} = -4mA$

$V_{OLmax} = 0.33V$ 所需假设: $V_{CC} = 4.5V$, $V_{IN} = V_{IH}$, $I_{OL} = 4mA$

$I_{OHmax} = -4mA$ 所需假设: $V_{CC} = 4.5V$, $V_{IN} = V_{IL}$, TTL负载

$I_{OLmax} = 4mA$ 所需假设: $V_{CC} = 4.5V$, $V_{IN} = V_{IH}$, TTL负载



3.31 不能在接触CMOS器件前与朋友握手

握手可能产生静电,之后触摸CMOS器件,静电会击穿和损坏MOS晶体管

3.32 转换时间受负载电容影响更大



$$\begin{aligned} 3.36 \Delta P_D &= (C_{PD} + C_L) \cdot (5^2 - 2.5^2) \cdot f \\ &= 18.75 (C_{PD} + C_L) \cdot f \end{aligned}$$

3.37. 滞后约为 $1.7 - 1.2 = 0.5V$

3.60 ~~$Z = \overline{A \vee (B \wedge C)} = A \wedge (\overline{B \vee C})$~~

$Z = \overline{A \wedge (B \vee C)} = A \vee (\overline{B \vee C})$

考虑使用或与非门来实现

  

3.6.8 CMOS输出为高电平时:

$$V_{out} = 5 - (5-2) \times \frac{200}{200+900} \approx 4.45V$$

CMOS晶体管输出为低电平时:

$$V_{out} = 2 \times \frac{100}{100+900} = 0.2V$$

由高电平到低电平时:

$$V_{out} = 4.45 \times e^{-\frac{t}{9 \times 10^{-9}}} + 0.2 \quad V$$

放电时, R_L 与 R_n 并联, $R = \frac{100 \times 900}{100+900} = 90\Omega$ (所以 RC_L 为 9×10^{-9} 秒)

$$t = -9 \times 10^{-9} \times \ln \frac{V_{out} - 0.2}{4.25}$$

$$t_{3.5} = 2.278 ns$$

$$t_{1.5} = 10.661 ns$$

$$\Delta t = t_{1.5} - t_{3.5} = 8.383 ns$$

~~3.6.1~~ 3.6.1节的结果为 $8.5 ns$, 二者相差不大

解释: 直流负载对转换时间影响不大



3.79 最低有效位转换频率为 16MHz

最高有效位转换频率为 $\frac{16\text{M}}{2^7} = \frac{1}{2^3}\text{MHz}$

8个输出位的动态功耗, 需要考虑每位位的转换频率

$$f = (1 + \frac{1}{2} + \frac{1}{2^2} + \dots + \frac{1}{2^7}) 16\text{MHz}$$

$$= \frac{2^7 + 2^6 + \dots + 2^0}{2^7} \cdot 16\text{MHz}$$

$$= \frac{2^8 - 1}{2^7} \cdot 16\text{MHz} = \frac{255}{8}\text{MHz}$$

